http://www.onlinebu.com

Total No. of Questions: 6

Total No. of Printed Pages :

EI-179

B.E. (Ind Sem.) (CGPA) Civil Engg. Examination-2015

BASIC ELECTRICAL & ELECTRONICS ENGG.

Paper: CE-203 Time Allowed: Three Hours Maximum Marks: 60

Note: Attempt all questions.

Attempt all part of a question in sequence.
Internal choice in each unit is given.

- Q.I Choose the correct answer-
 - (i) When three coil are connected in star across 400 V supply. The each coil have resistance of 10Ω and inductance of 0.02 H. The line current will be
 - (a) 5.9 A lagging
 - (b) 5.9 A leading
 - (¢) 5.9√3 lagging
 - (d) 5.9√3 leading

El-179

P.T.O.

http://www.onlinebu.com

(2)

- (ii) The real power absorbed in each phase of circuit is—
 - (a) $\sqrt{3} V_{\rho} I_{\rho} \cos \phi$
 - (b) $\sqrt{3} V_L I_C \cos \phi$
 - (c) $V_p I_p \cos \phi$
 - d) $\sqrt{3} V_L I_L$
- (iii) The law relates to emf and voltage drops in a circuit at any closed path—
 - (a) $\Sigma E \Sigma IR = 0$
 - (b) $\Sigma E + \Sigma IR = 0$
 - (c) No option is true
- (iv) The unit of m.m.f. in a magnetic circuit is given by—
 - (a) Weber
 - (b) Amp
 - (c) Amptum -
 - (el) Wb/m²

EI-179

Contd.

- (v) The power factor angle of a purely inductive circuit is-
- (b) $\phi = +90^{\circ}$
- (c) $\phi = 45^{\circ}$
- (vi) The hystersis loss in case of transformer is proportional to-
 - (a) $P_{\nu} \alpha f$
- (b) $P_c \alpha \sqrt{f}$
- (c) $P_e \propto f^2$ (d) $P_e = f^{1.5}$
- (vii) The condition of maximum efficiency of a transformer is-
 - ·(a) Copper losses < Iron losses
 - Copper losses > iron losses
 - (c) Copper losses = iron loss
 - (d) Copper losses should remain constant
- (viii) The Torque developed in D. C. motor is-

 - (c) $T\alpha \phi . I_{\alpha}$

P.T.O.

http://www.onlinebu.com

(4)

- (ix) The speed of a d.c. motor is-
 - (a) Nα φ


 - (c) N= constant
 - (d) $N \alpha \phi^{1.5}$
- (x) The relation between frequency, speed and number of poles is given by-

(a)
$$N_S = \frac{120 f}{P}$$

(b)
$$f = \frac{PN_{S}}{120}$$

(c)
$$n_S = \frac{2f}{P}rps$$

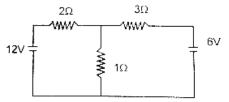- (d) Any one (a), (b) or (c)
- (a) Solve the network by Mesh current method-5



(b) State and explain KCL & KVL.

or

(a) State and explain superposition theorem. 4


El-179

Contd.

5

http://www.onlinebu.com

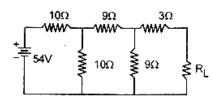(b) Determine the current flowing through RL when load resistance is 3Ω.



Q.III (a) Define the following terms—

4

- i) Magnetic flux
- (ii) m.m.f.

http://www.onlinebu.com

- (iii) Permeability
- (iv) Reluctance
- (b) Give the analogy between electric and magnetic circuits.

or

- (a) What do you understand by magnetic leakage and fringing.
- (b) Define hystersis loop of magnetic material. 6
- Q.IV (a) Derive relation between line voltage and phase voltage of three phase star connection.

El-179

P.T.O.

http://www.onlinebu.com

(6)

- (b) Define the following terms-
 - (i) Frequency
 - (ii) Amplitude
 - (iii) Phase and phase difference

Of

- (a) Explain two Wattmeter method for measurement of power in a 3φ circuit.
- (b) A choke coil has a resistance of 10Ω and inductance of 0.05H is connected in series. with 100μF. The whole circuit is connected 200 Volts, 50 Hz-supply. Calculate— 5
 - (i) Impedance
 - (ii) Current
 - (iii) Powerfactor
- Q.V (a) Explain the working principle of a reformer. 5
 - (b) A transformer has a maximum efficiency of 98% at 15KVA at unity p.f. It is loaded as follows—

12 hrs

2 kw at pf = 0.5

6 hrs

6 kw at pf = 0.8

6 hrs

18 kw at pf = 0.9

Calculate all day efficiency of transformer.

El-179

Contd.

(7)

Q.VI (a) Explain the constructional features of a D. C.

Machine. 5

(b) Explain diagram of self excited dc generator.5

or

- (a) Describe various methods of speed control of d.c. moters.
- (b) Draw and explain characteristics of d.c., shunt motor.

://www.onlinebu.com

El-179